

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5459]-182

S.E. (Computer Engineering) (I Sem.) EXAMINATION, 2018

DIGITAL ELECTRONICS AND LOGIC DESIGN

(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Attempt Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6,
Q. 7 or Q. 8.

(ii) Neat diagram must be drawn wherever necessary.

(iii) Assume suitable data, if necessary.

1. (a) How will you implement full-adder using half-adder ? Explain the circuit diagram. [6]
- (b) How lockout condition in counter is avoided ? [2]
- (c) Draw and explain Ring counter using JK flip-flop (Timing Diagram is expected). [4]

Or

2. (a) Design full Subtractor using multiplexer IC 74151. [4]
- (b) Compare synchronous and asynchronous counter. [2]
- (c) Simplify the following function using Quine-McCluskey minimization technique :

$$Y(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14). \quad [6]$$

P.T.O.

3. (a) Design an ASM chart for 2-bit UP counter using mode control line. [6]

When M = 1 UP counting

When M = 0 remain in same state.

- (b) Implement the following function using PAL :
 $F1(A, B, C, D) = \Sigma m(1, 3, 4, 6, 9, 12, 14)$
 $F2(A, B, C, D) = \Sigma m(1, 2, 3, 7, 12, 15).$ [4]
- (c) Define PLD. Mention different types of PLD. [2]

Or

4. (a) Write VHDL code full adder using behavioural style of modeling. [4]
- (b) Explain entity declaration for 4 : 1 multiplexer having enable line. [2]
- (c) Design BCD to Excess-3 code converter using PLA. [6]
5. (a) Draw three input standard TTL NAND gate and explain its operation. [5]
- (b) Explain the interfacing of TTL and CMOS : [8]
- (i) CMOS driving TTL
- (ii) TTL driving CMOS.

Or

6. (a) Draw and explain wired AND gate in detail. [5]
- (b) Explain the characteristics of digital IC. [4]
- (c) Explain with a neat diagram CMOS NOR gate. [4]

7. (a) Explain addressing modes of 8051 with example (any *three*) : [6]
(b) List any *eight* applications of microcontroller 8051. [4]
(c) Explain the following pins of 8051 : [3]

(i) RXD

(ii) $\overline{\text{PSEN}}$

(iii) $\overline{\text{EA}}$.

Or

8. (a) State the registers used in Timer/counter operation. Explain TMOD register. [5]
(b) Explain the following instructions with respect to microcontroller 8051 and give example of each : [8]

(i) MUL

(ii) L JUMP

(iii) SWAP

(iv) PUSH.